

68000 Interface Timing Diagrams

- **Outline**

- 68000 Read Cycle
- 68000 Write Cycle

- **Goal**

- Understand 68000 bus cycles
- Learn how to attach memory, peripherals to CPU

- **Reading**


- *Microprocessor Systems Design*, Clements, Ch. 4


68000 Read Cycle


- **68000 read word from memory**
- **68000 acts as bus master**
 - initiates read
- **Memory acts as bus slave**
 - responds to master requests
- **Memory-mapped I/O**
 - “memory” can really be peripheral device
- **Interlocked handshaking between master and slave**
 - master uses R/~W, AS*, UDS*, LDS* to tell memory that address is present
 - slave uses DTACK* to tell CPU that data is ready
- **A 68000 memory access takes a minimum of eight clock states numbered from clock states S0 to S7**

Timing Diagrams

- **Not to scale - relationships more important**
- **Typically do not care about data/address signal values**
- **Do care about control signal values**
- **Voltage sensing**
 - V_{ol} - maximum logical zero voltage on output
 - V_{oh} - minimum logical one voltage on output
 - V_{il} - maximum logical zero voltage on input
 - V_{ih} - minimum logical one voltage on input
- **Time delays measured from reference voltage**
 - 50%, 10%, 90% of V_{dd}

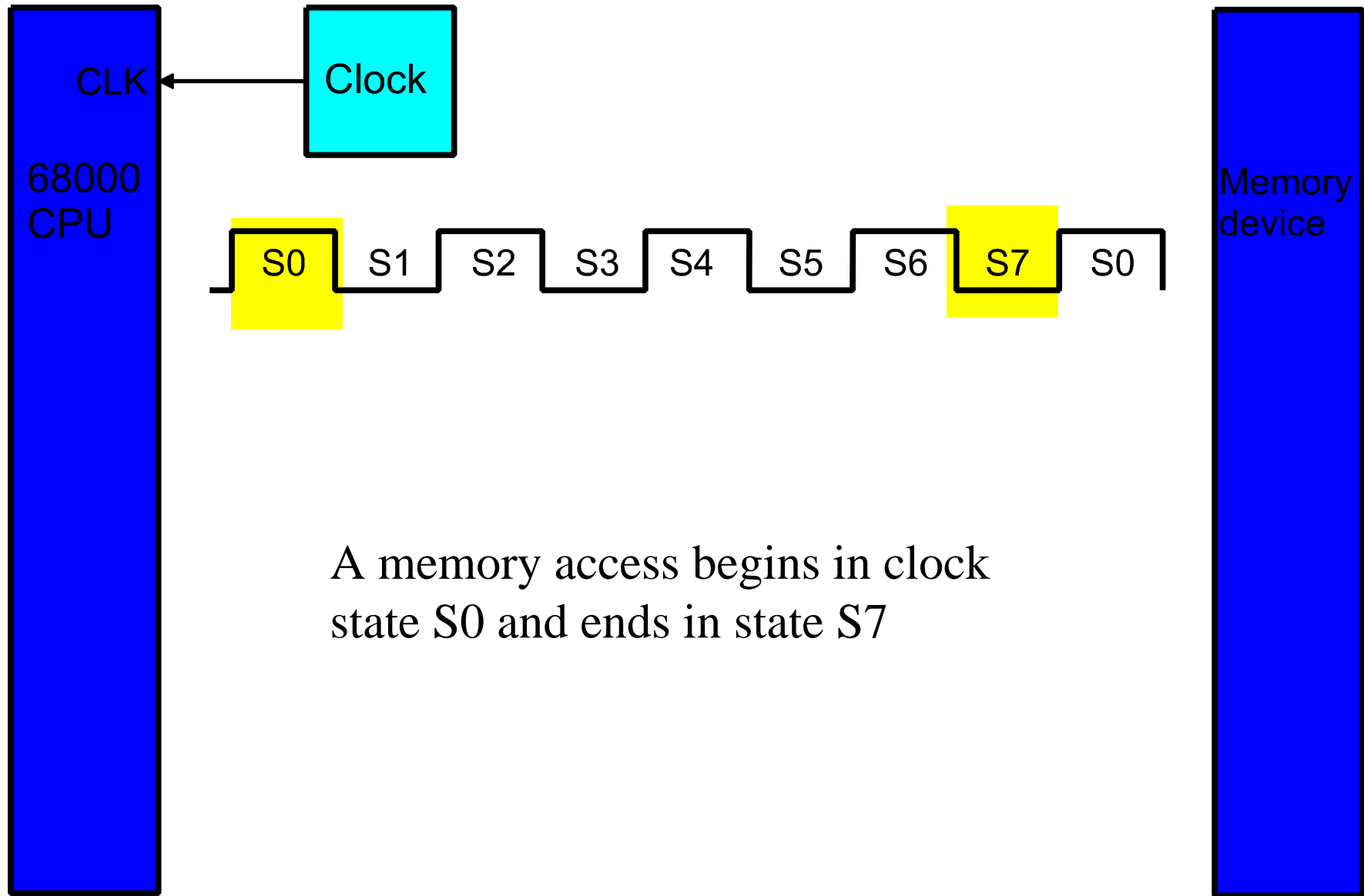


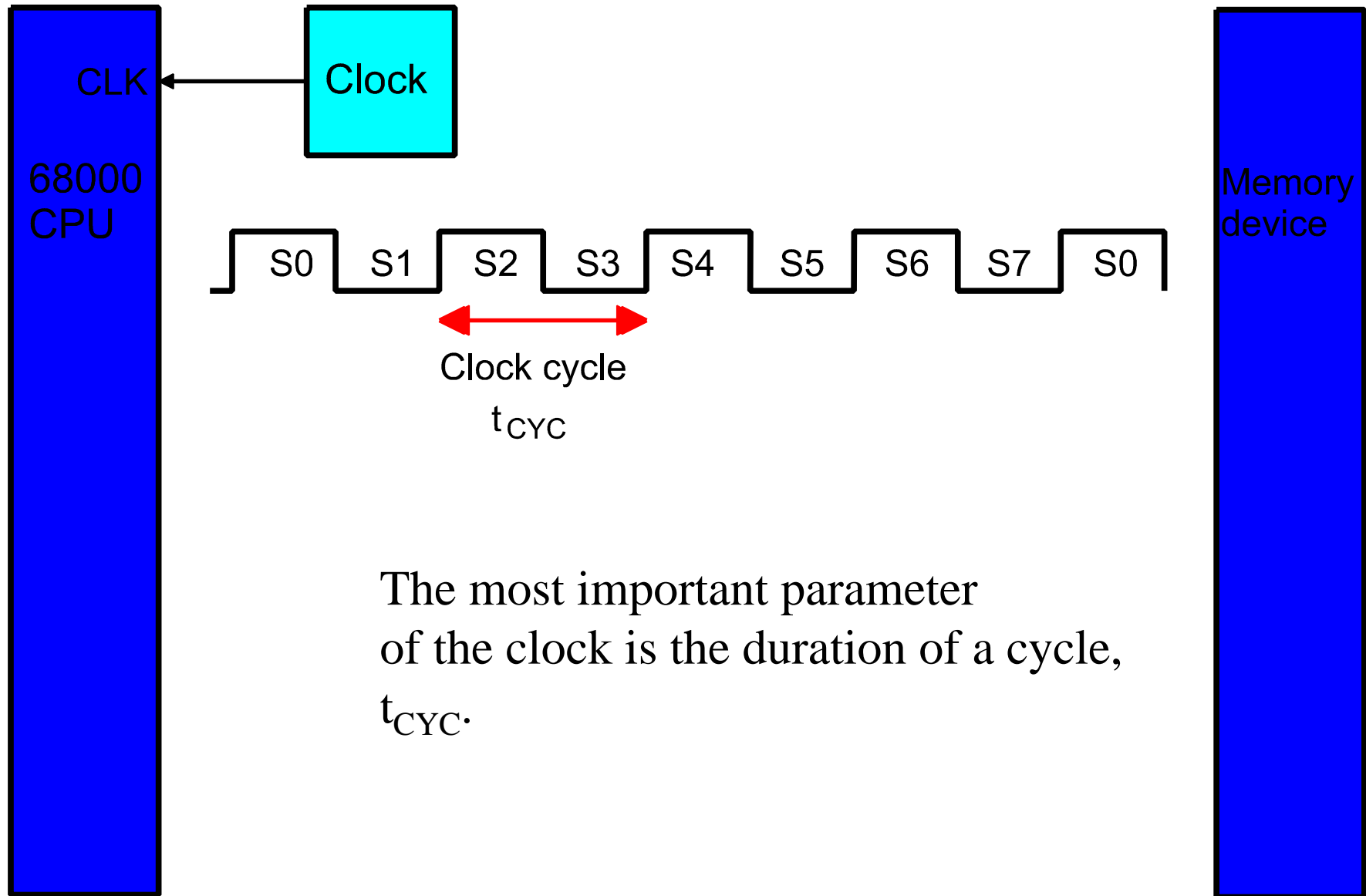


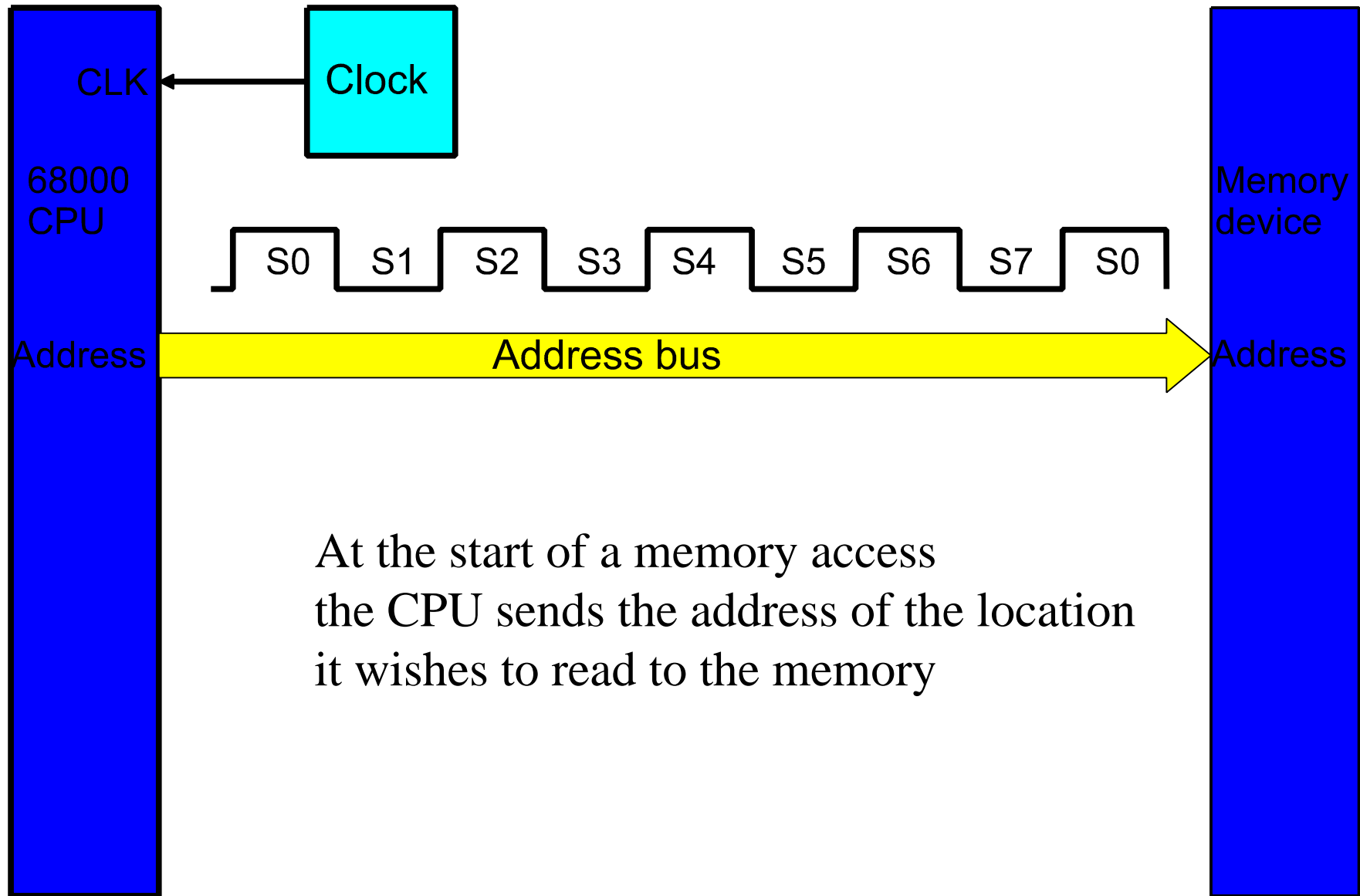

Address Timing

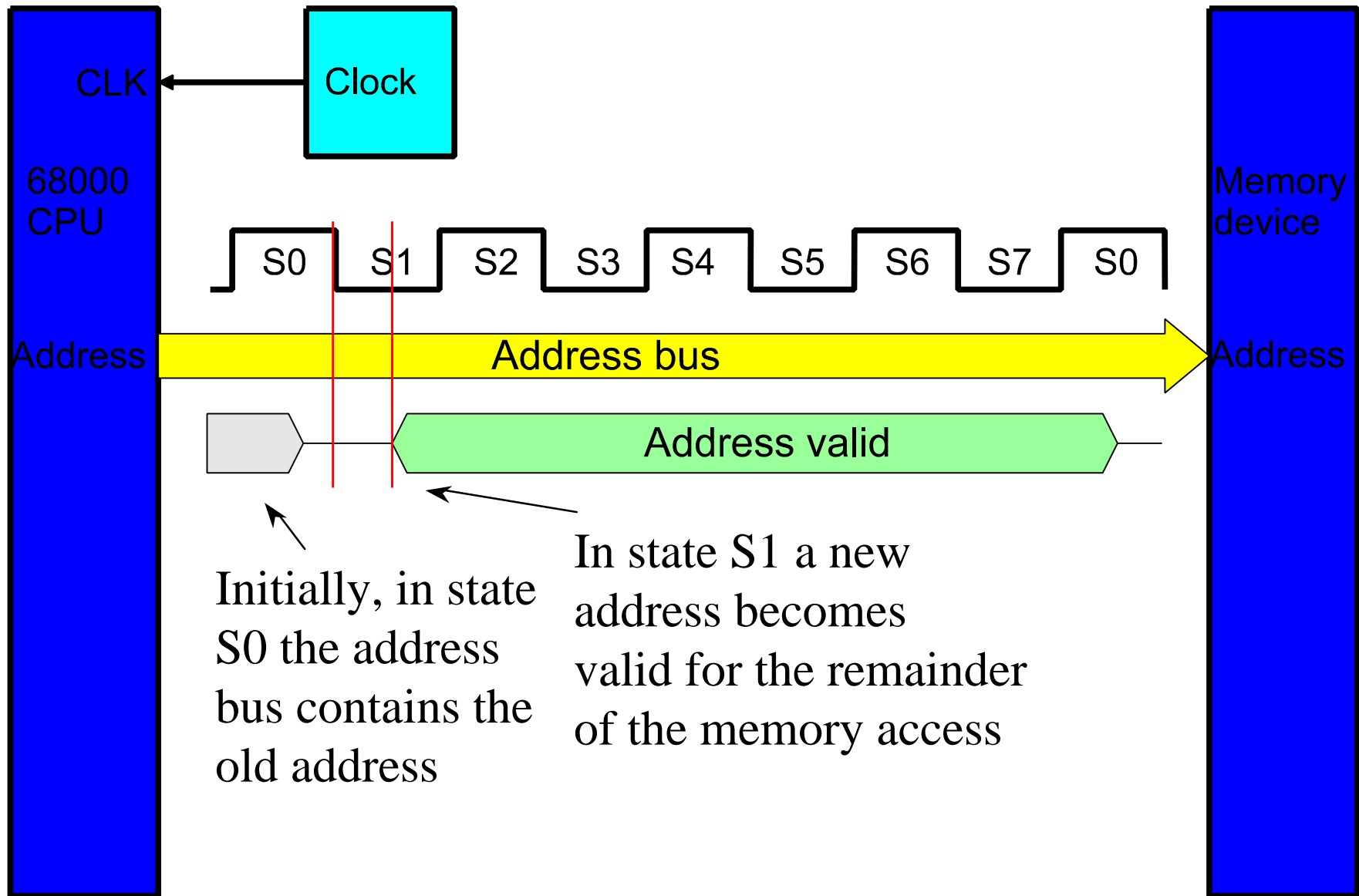
- **We are interested in when the 68000 generates a new address for use in the current memory access**
- **The next slide shows the relationship between the new address and the state of the 68000's clock**




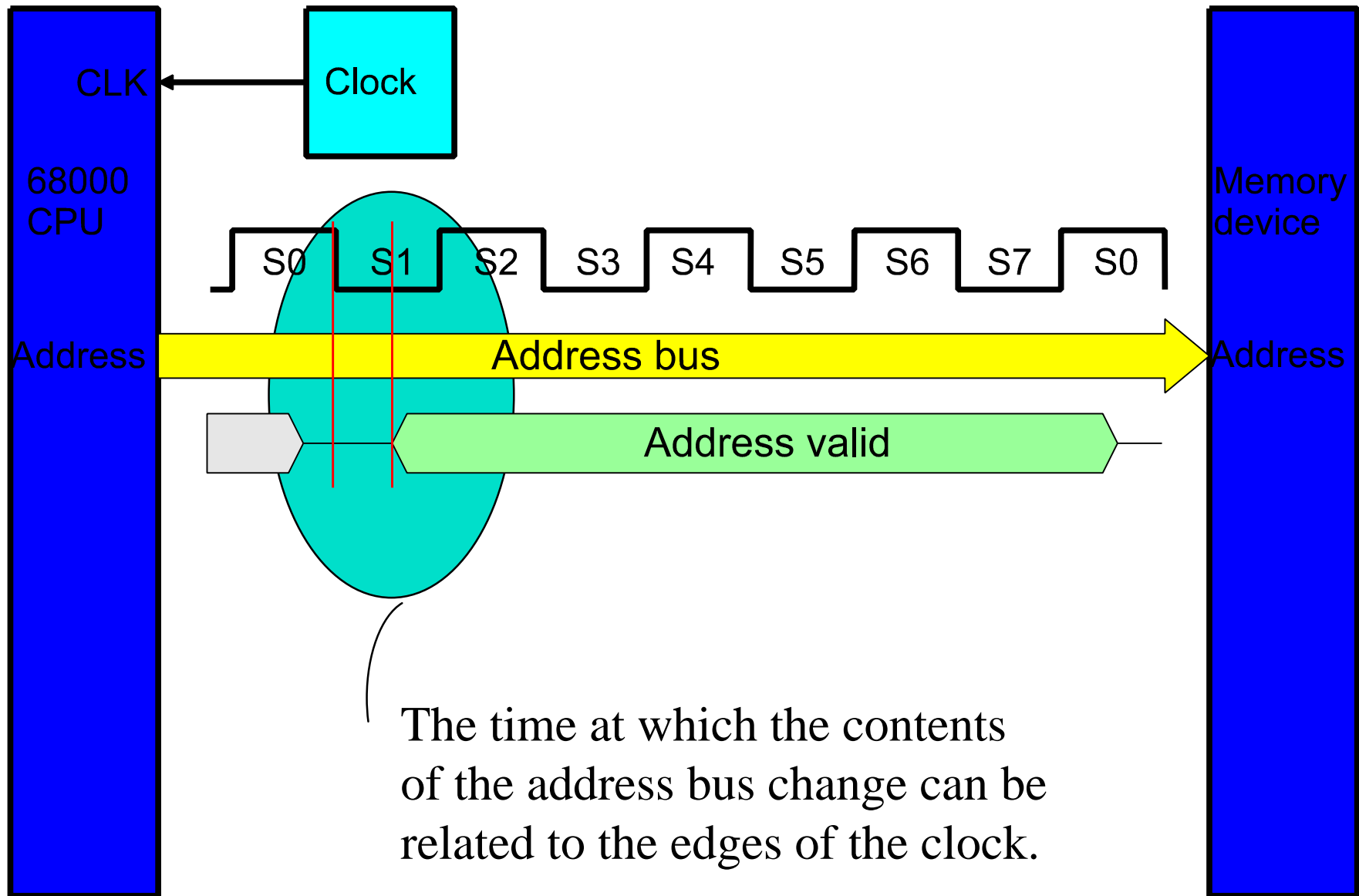


Address Timing

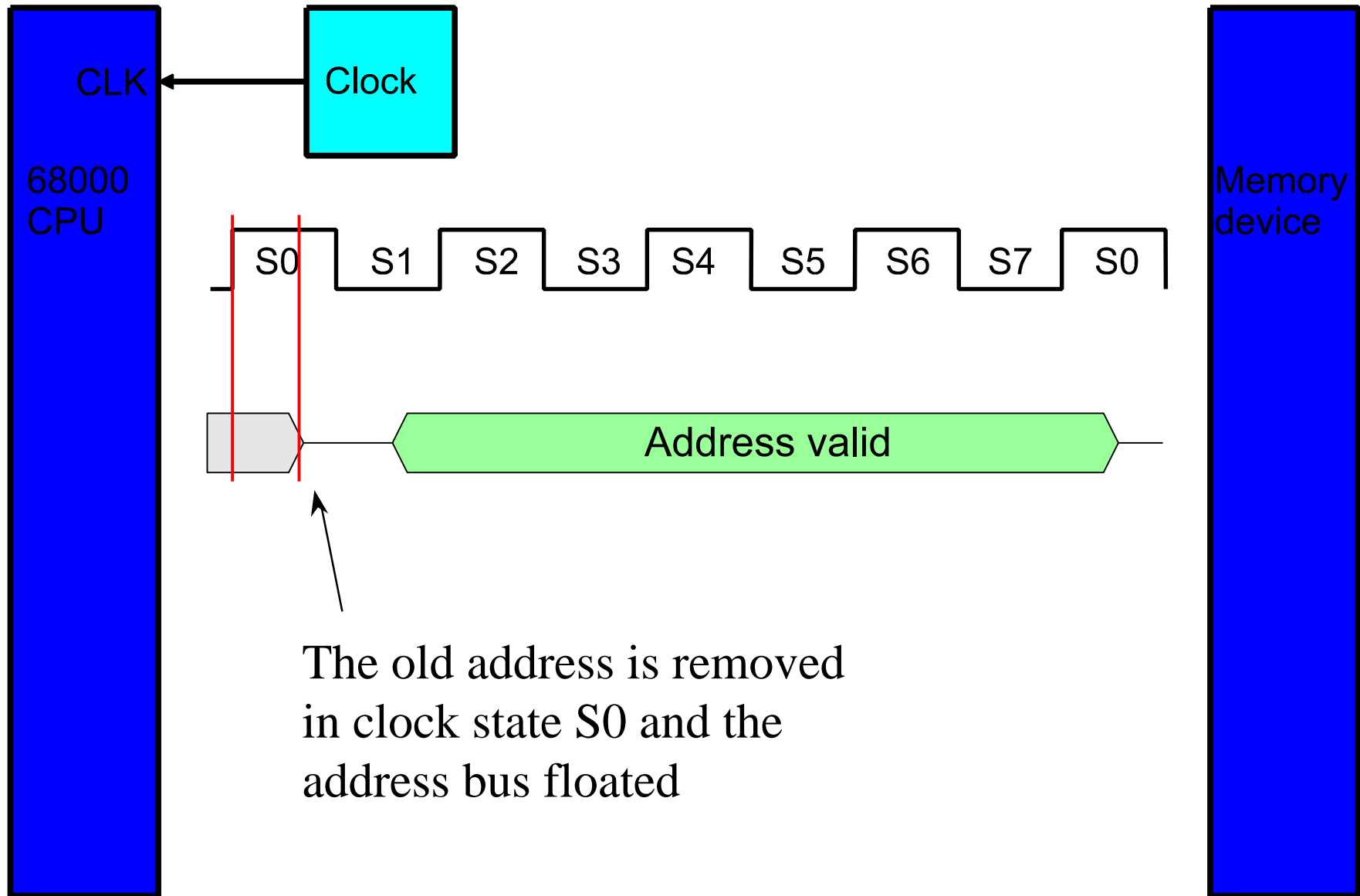- **Let's look at the sequence of events that govern the timing of the address bus**
- **The “old” address is removed in state S0**
- **The address bus is floated for a short time, and the CPU puts out a new address in state S1**




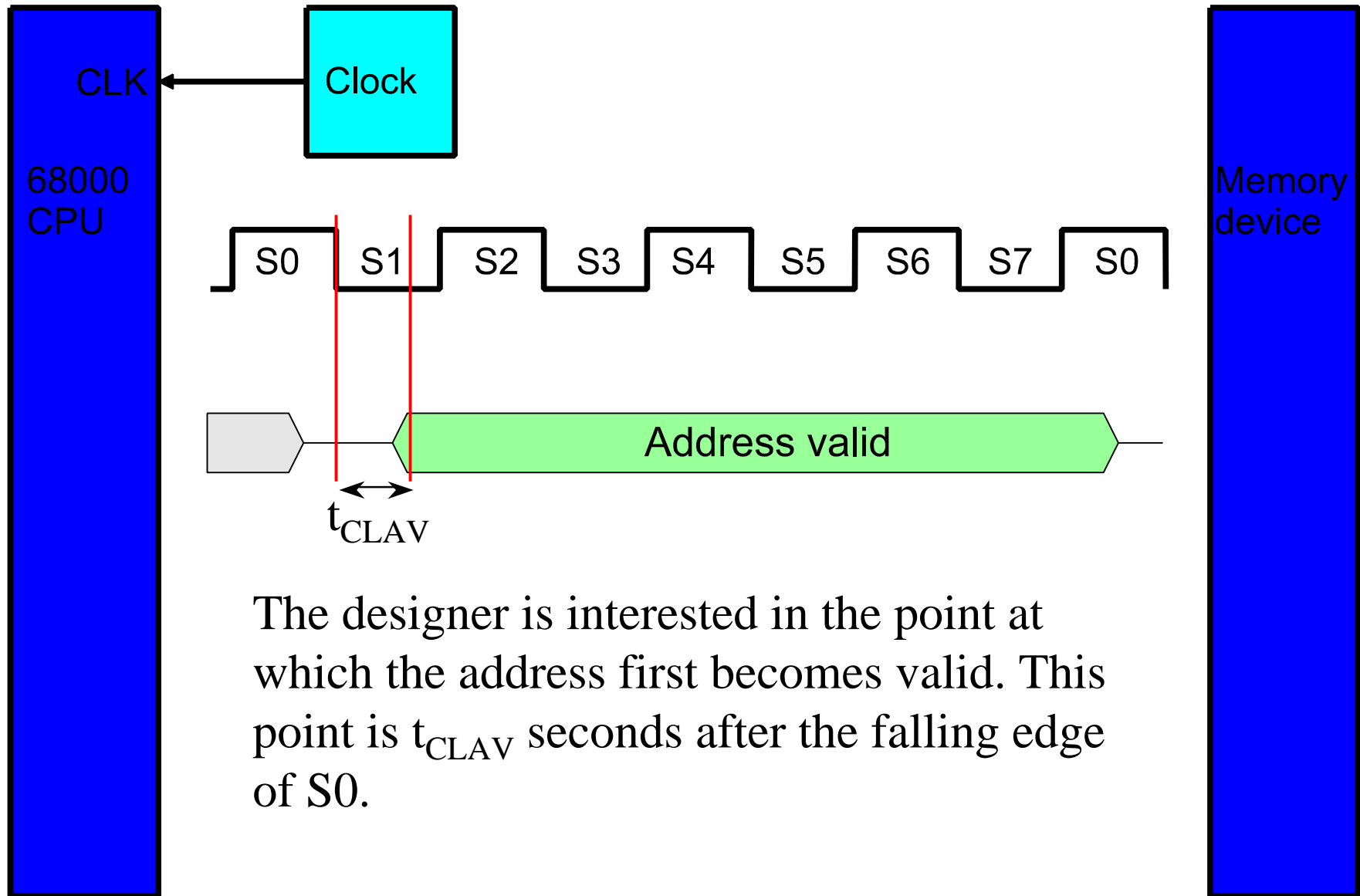


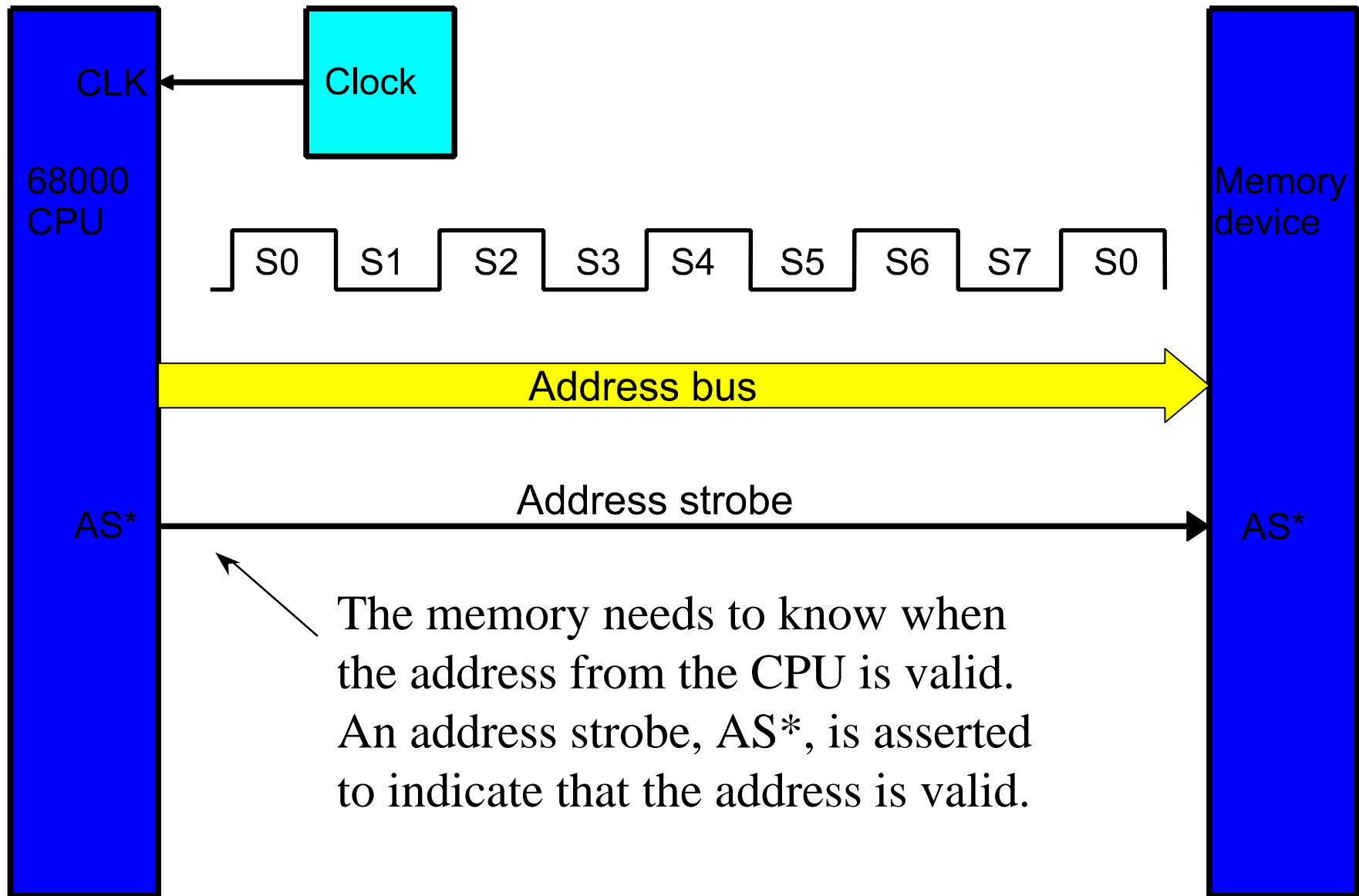

Address and Address Strobe

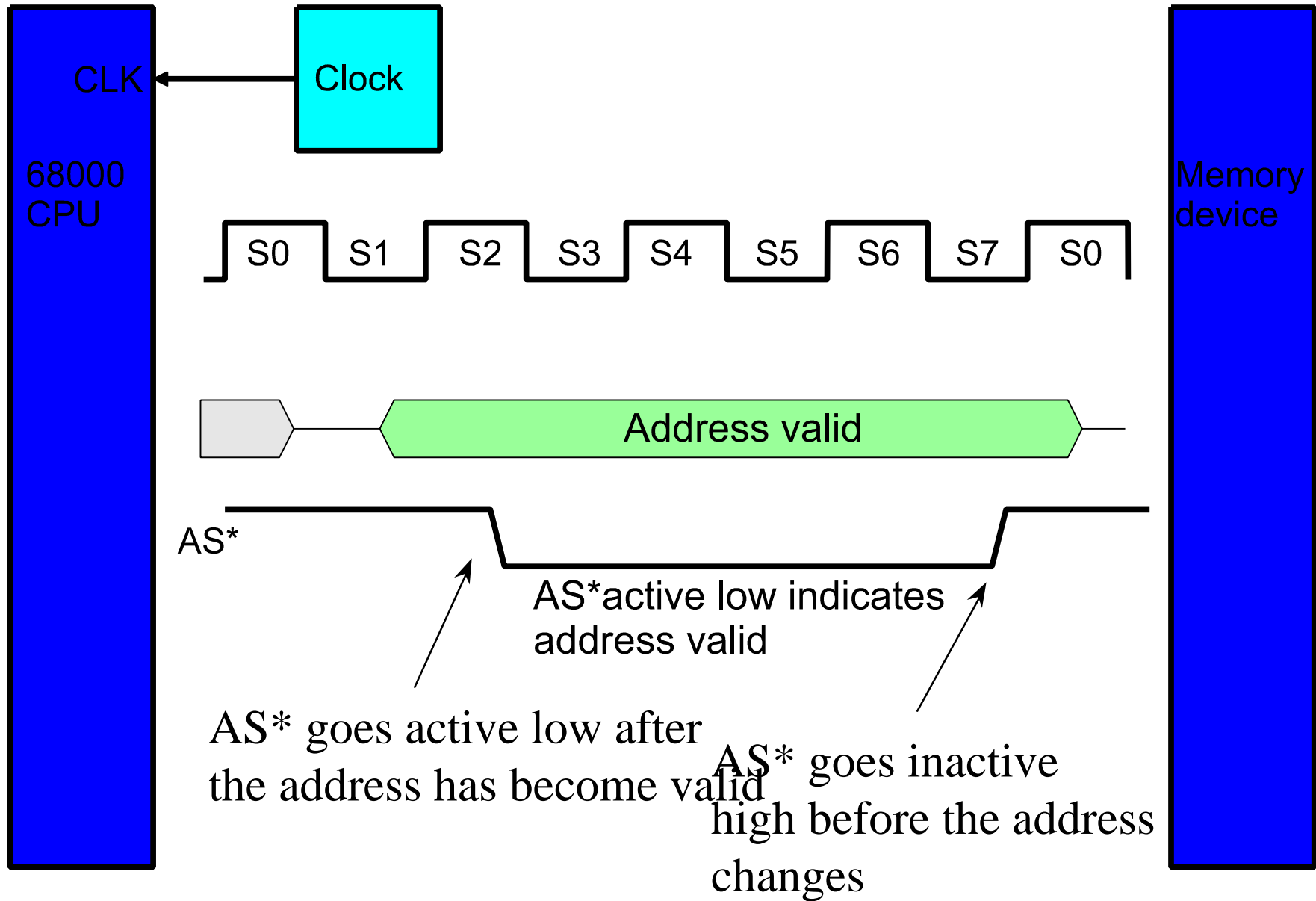
- We are interested in the relationship between the time at which the address is valid and the time at which the address strobe, AS^* , is asserted
- When AS^* is active-low it indicates that the address is valid
- We now look at the timing of the clock, the address, and the address strobe



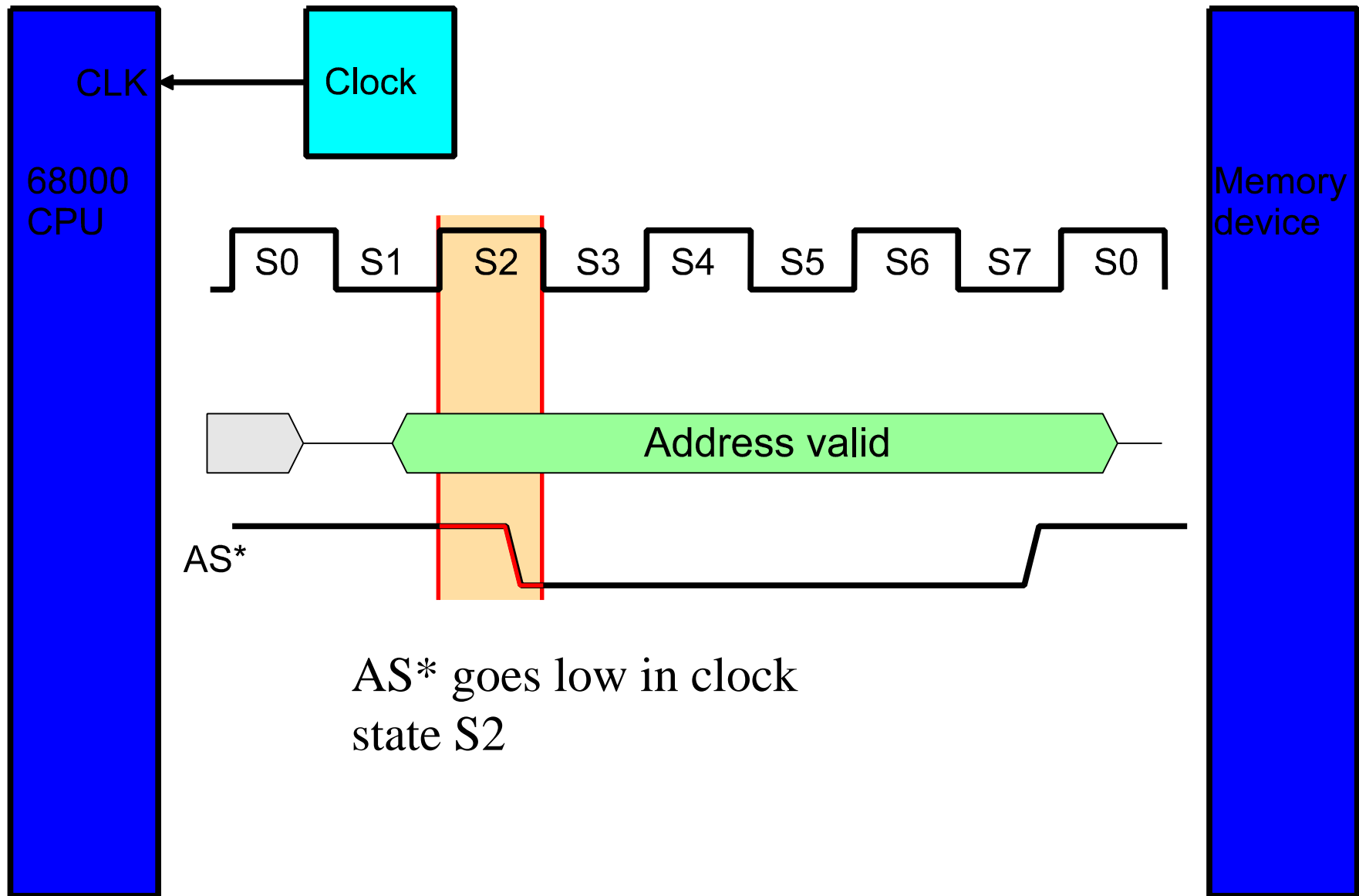

The Data Strobes

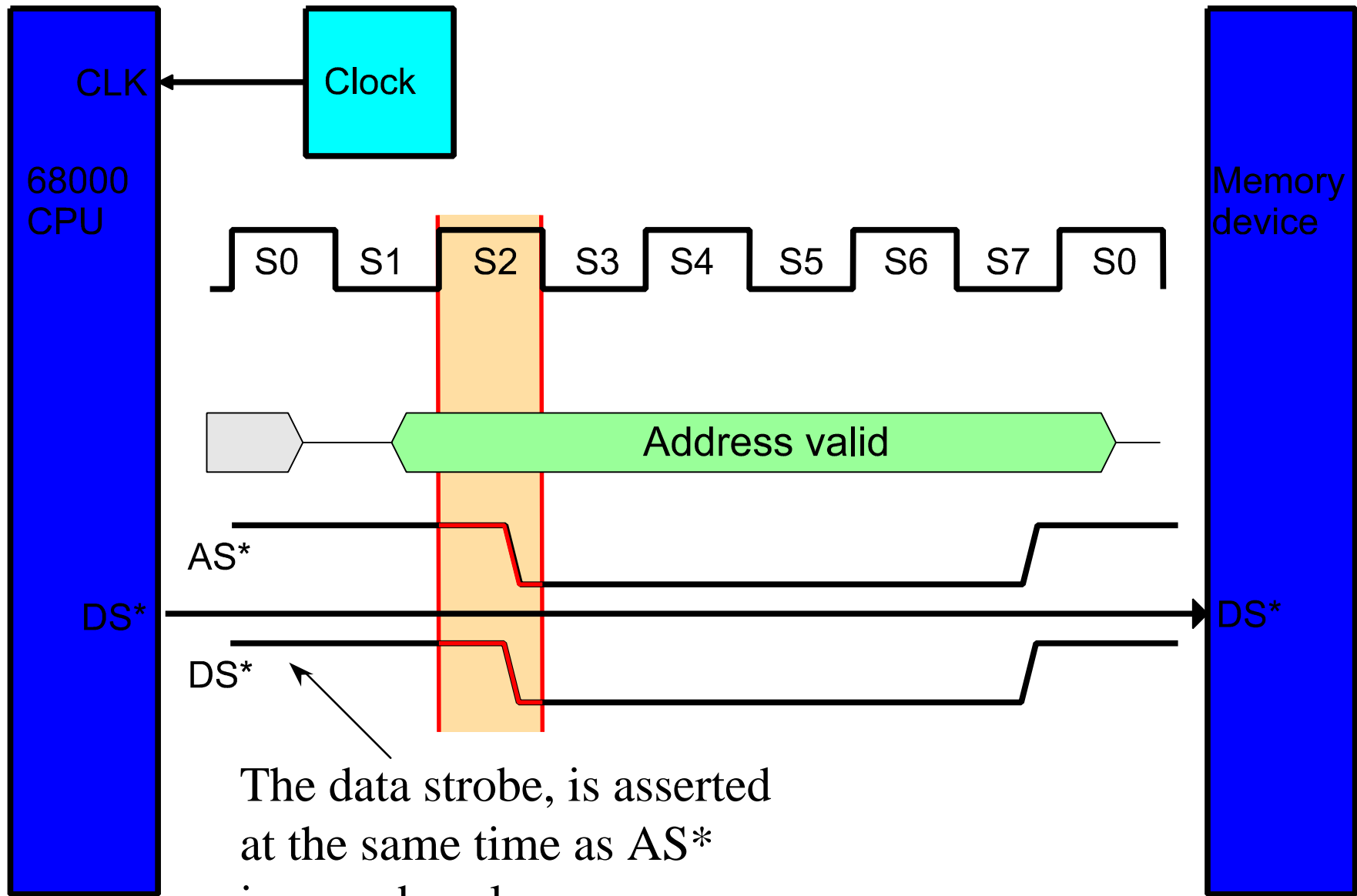
- The 68000 has two data strobes LDS* and UDS*. These select the lower byte or the upper byte of a word during a memory access
- To keep things simple, we will use a single data strobe, DS*
- The timing of DS* in a read cycle is the same as the address strobe, AS*



The data strobe, is asserted
at the same time as AS*
in a read cycle


The Data Bus

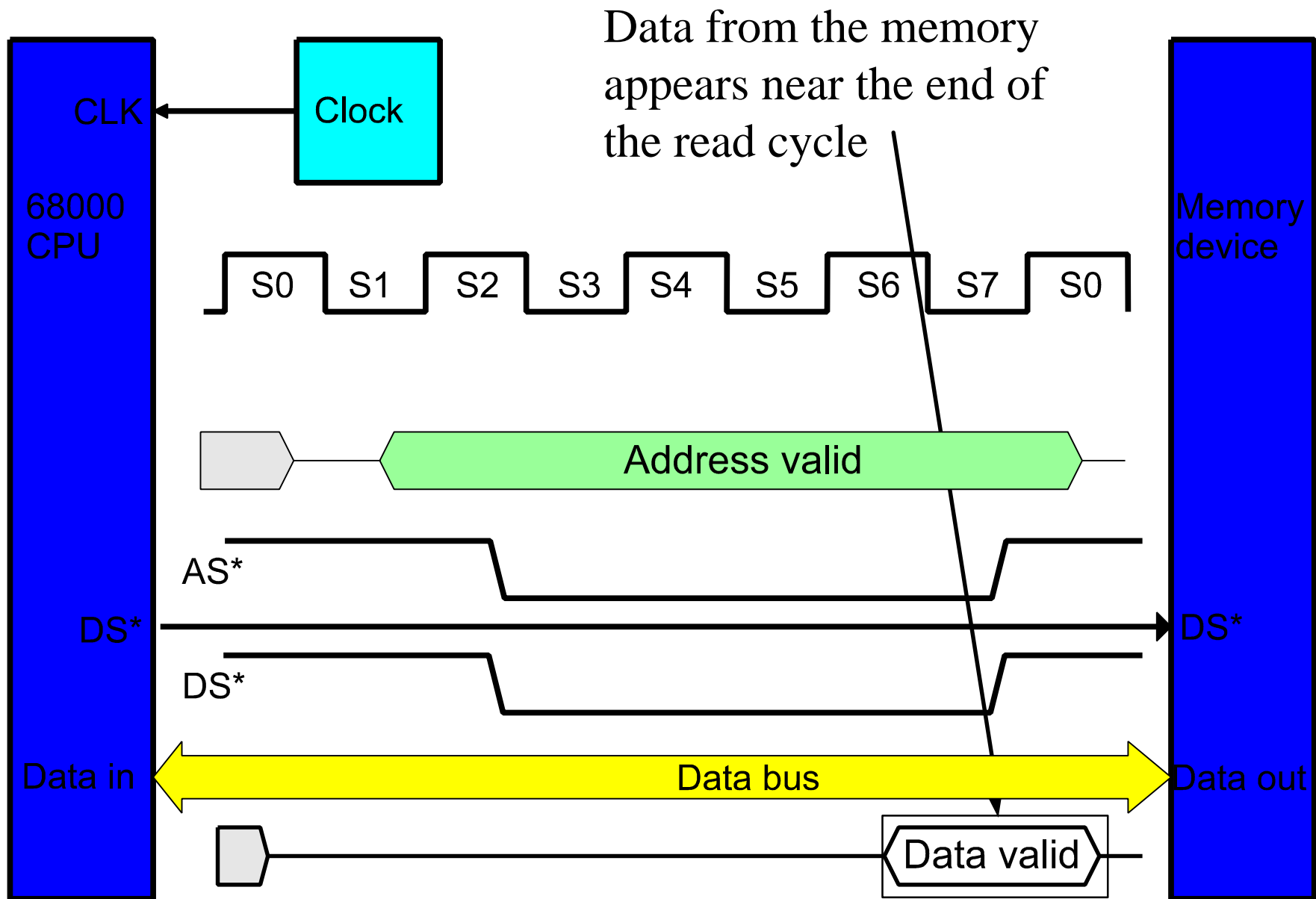
- **During a read cycle the memory provides the CPU with data**
- **The next slide shows the data bus and the timing of the data signal**
- **Note that valid data does not appear on the data bus until near the end of the read cycle**




Analyzing the Timing Diagram

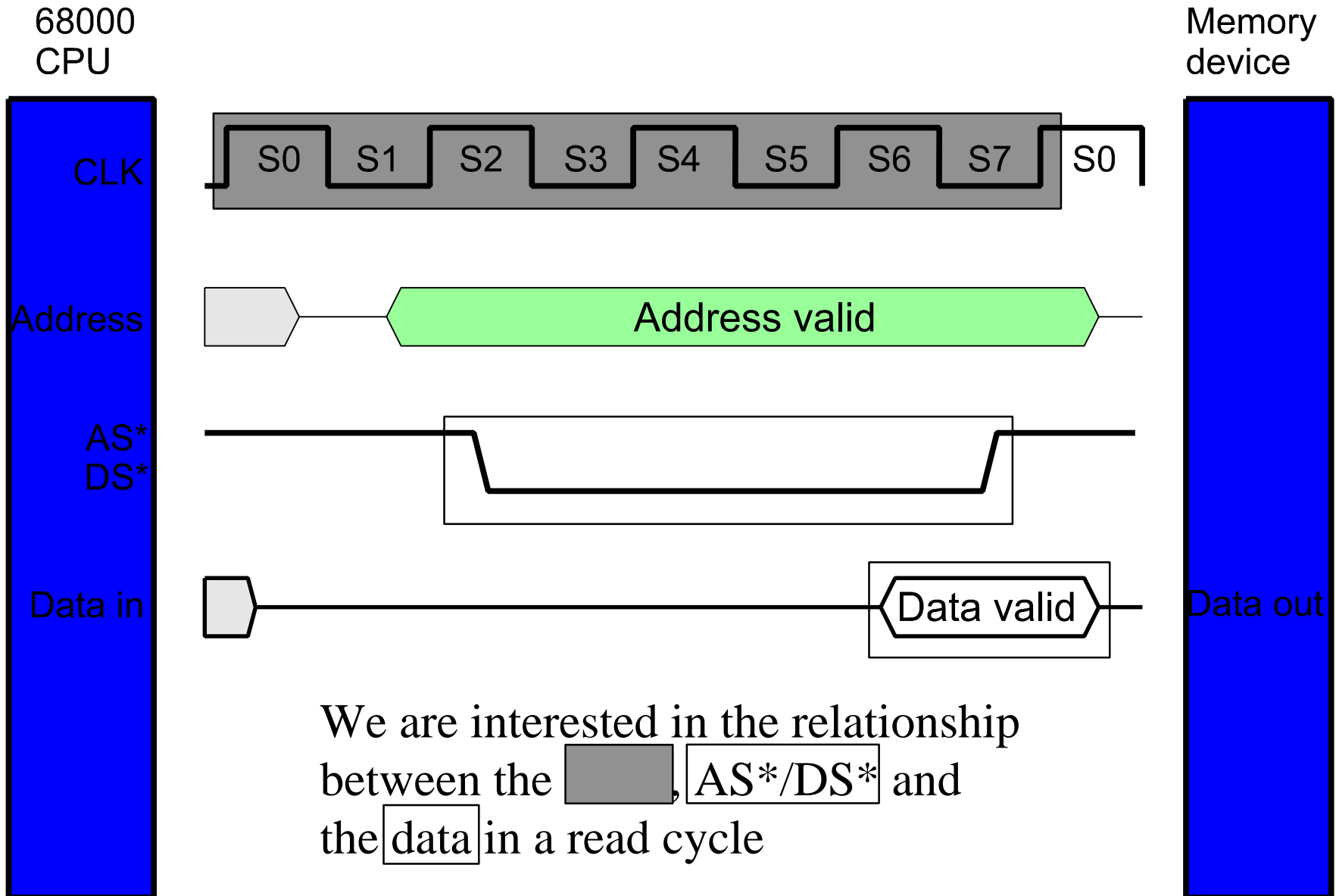- **We are going to redraw the timing diagram to remove clutter**
- **We aren't interested in the signal paths themselves, only in the relationship between the signals**




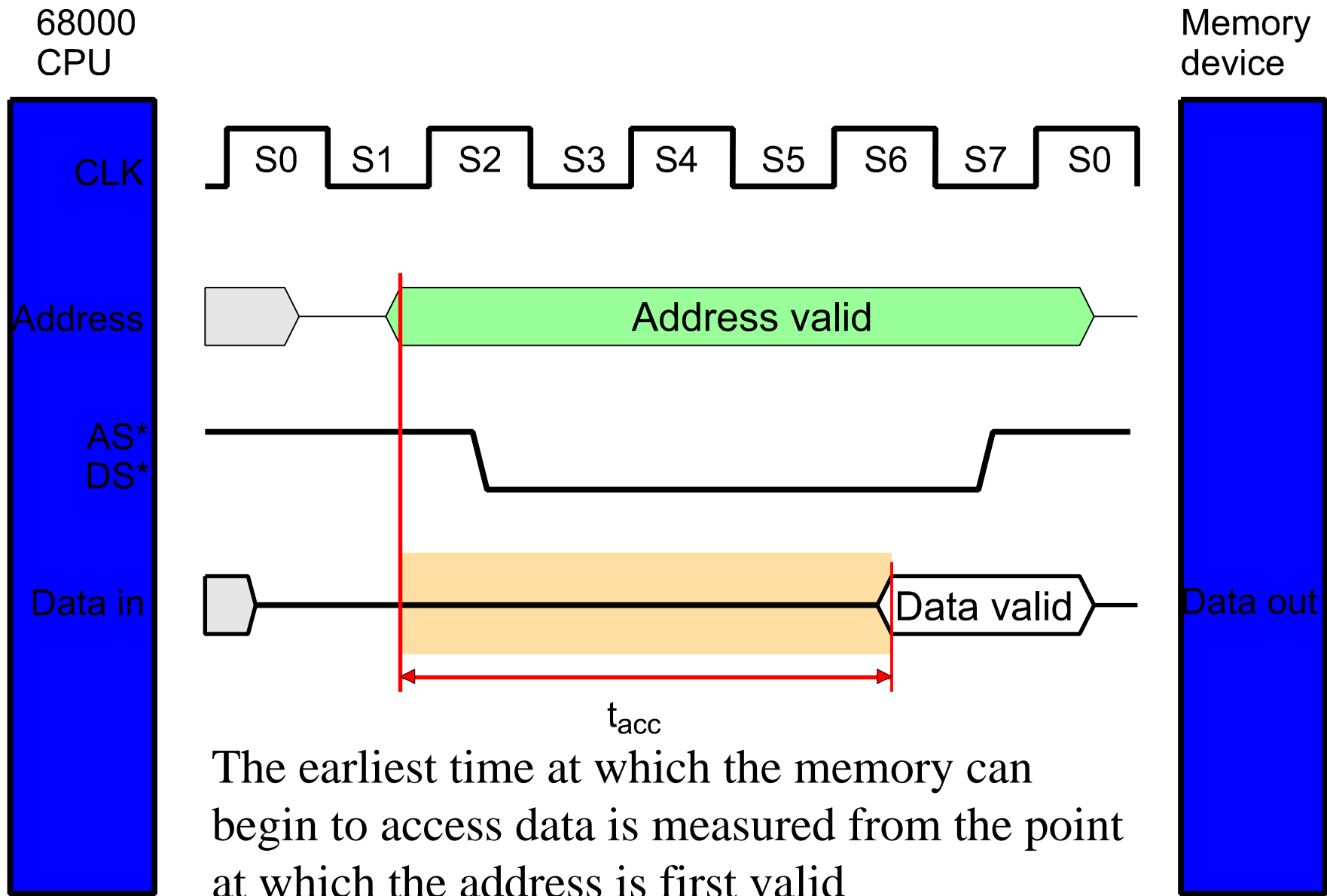


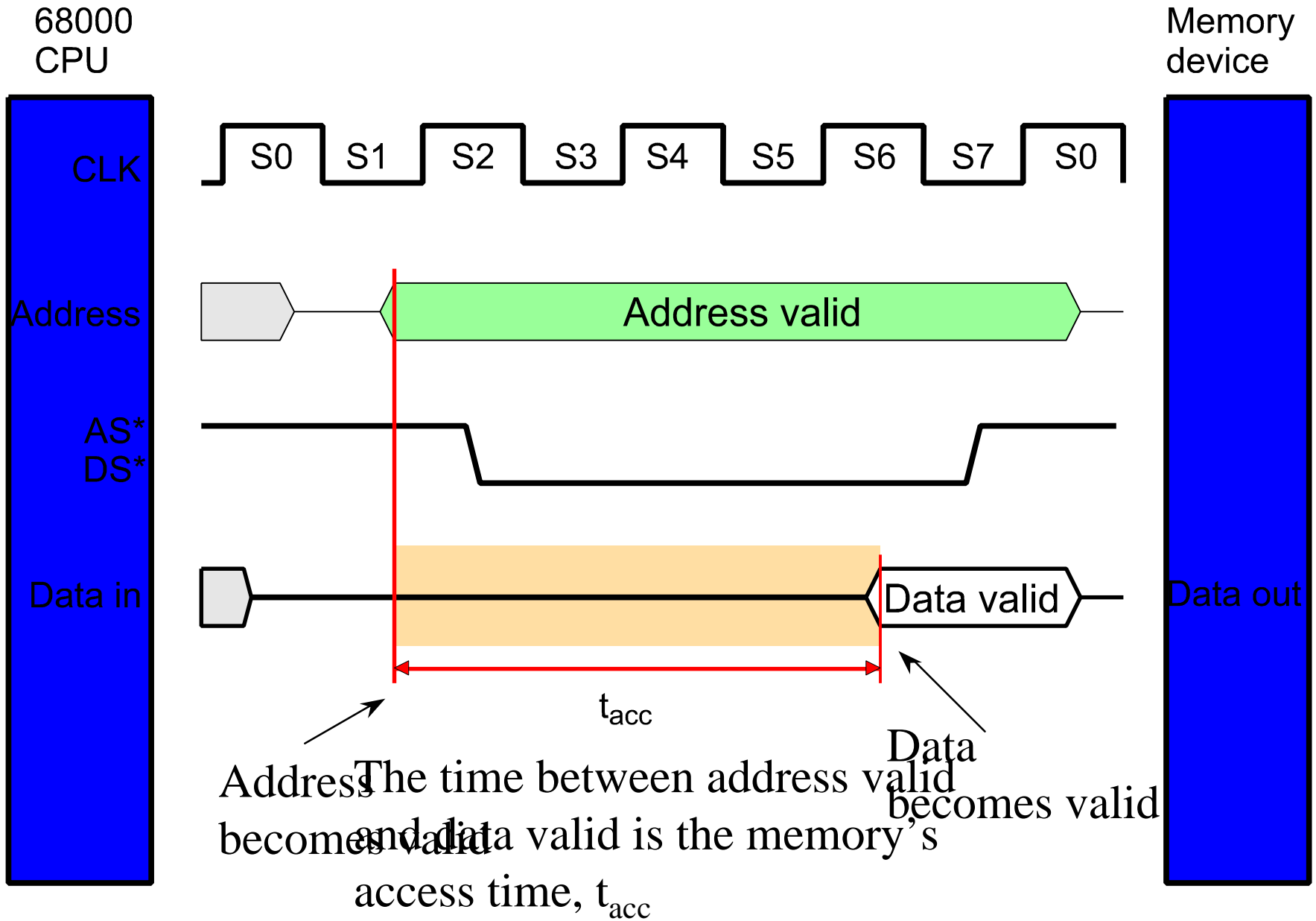



Calculating the Access Time

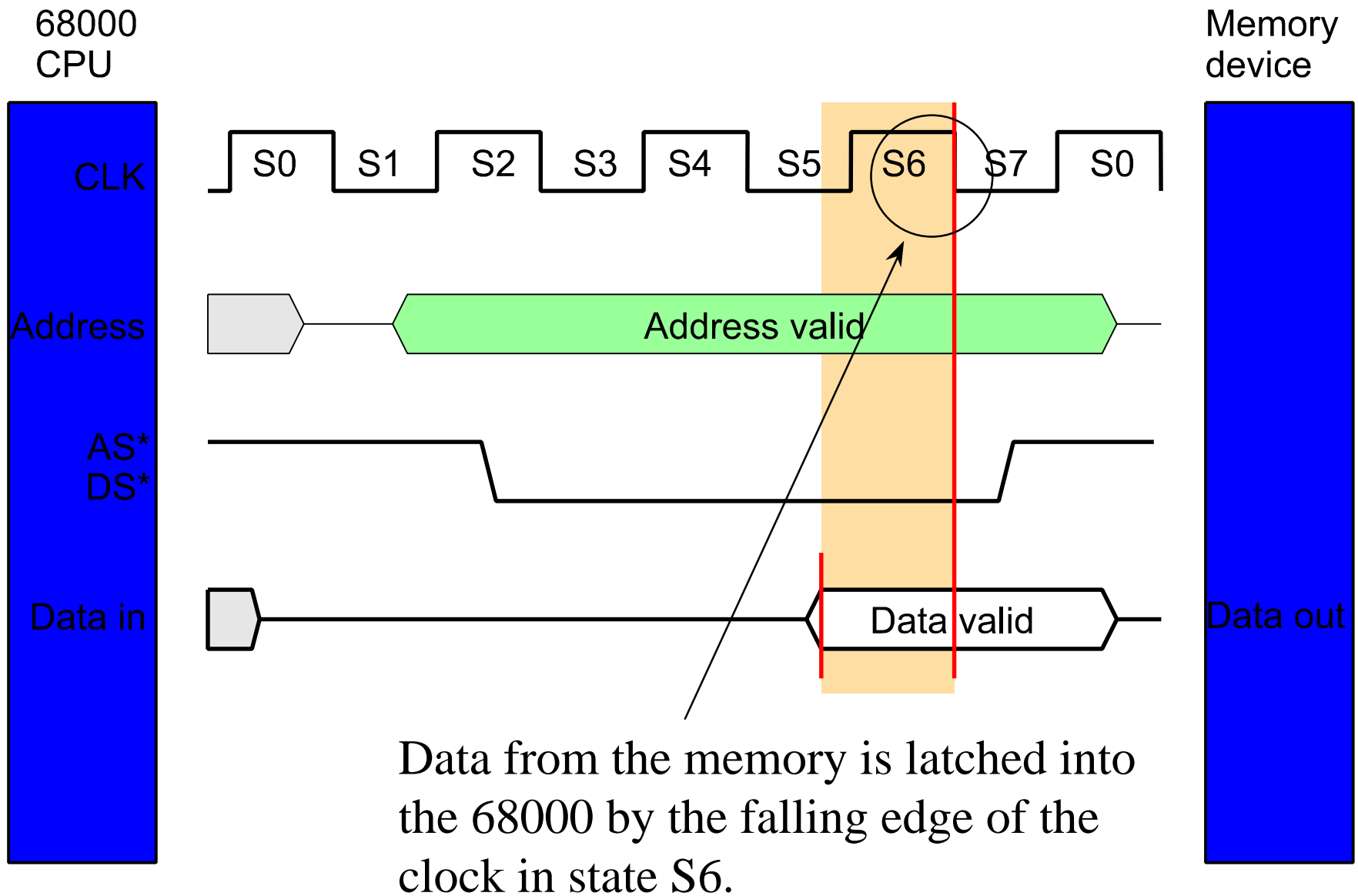
- We need to calculate the memory's access time
- By knowing the access time, we can use the appropriate memory component
- Equally, if we select a given memory component, we can calculate whether its access time is adequate for a particular system




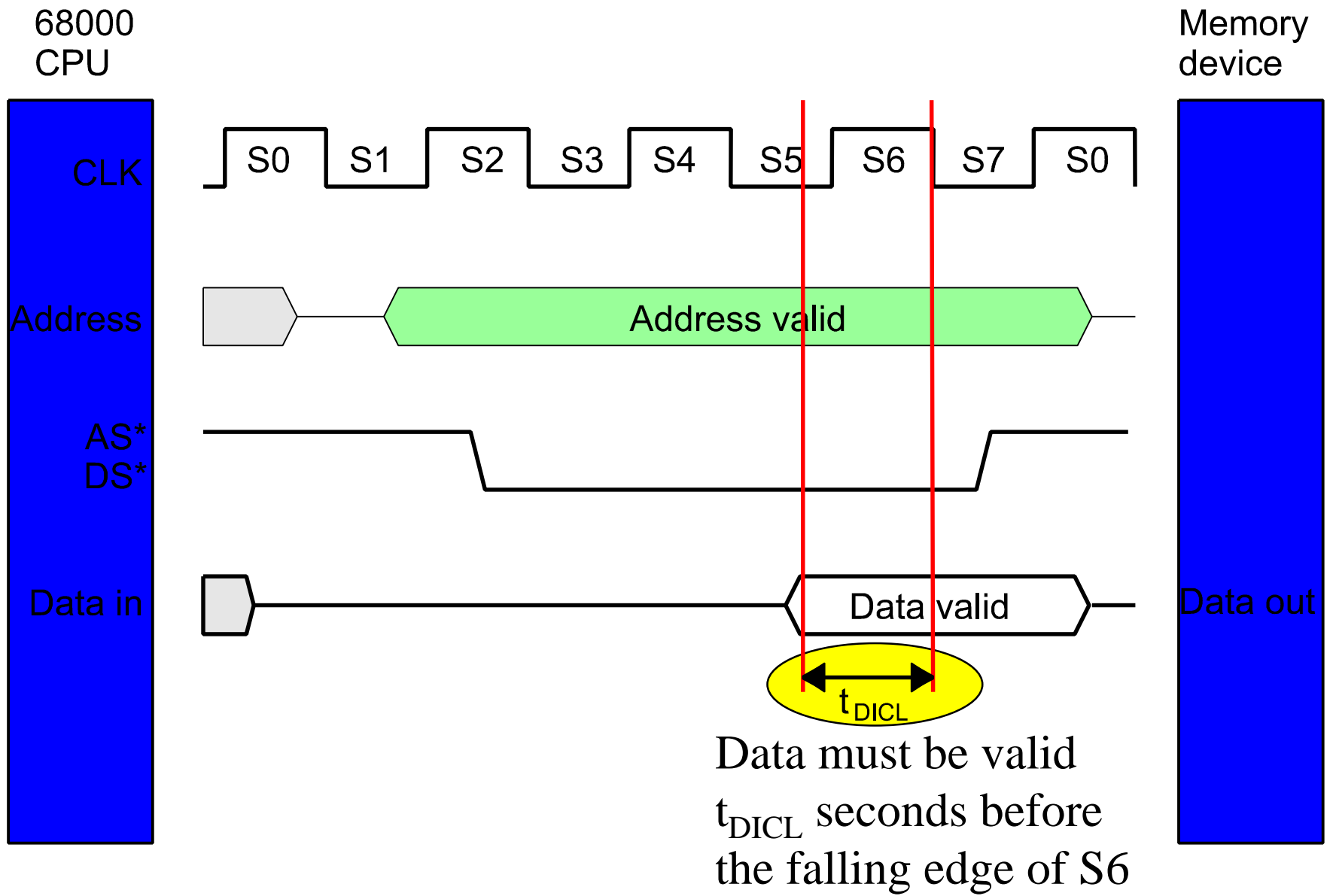


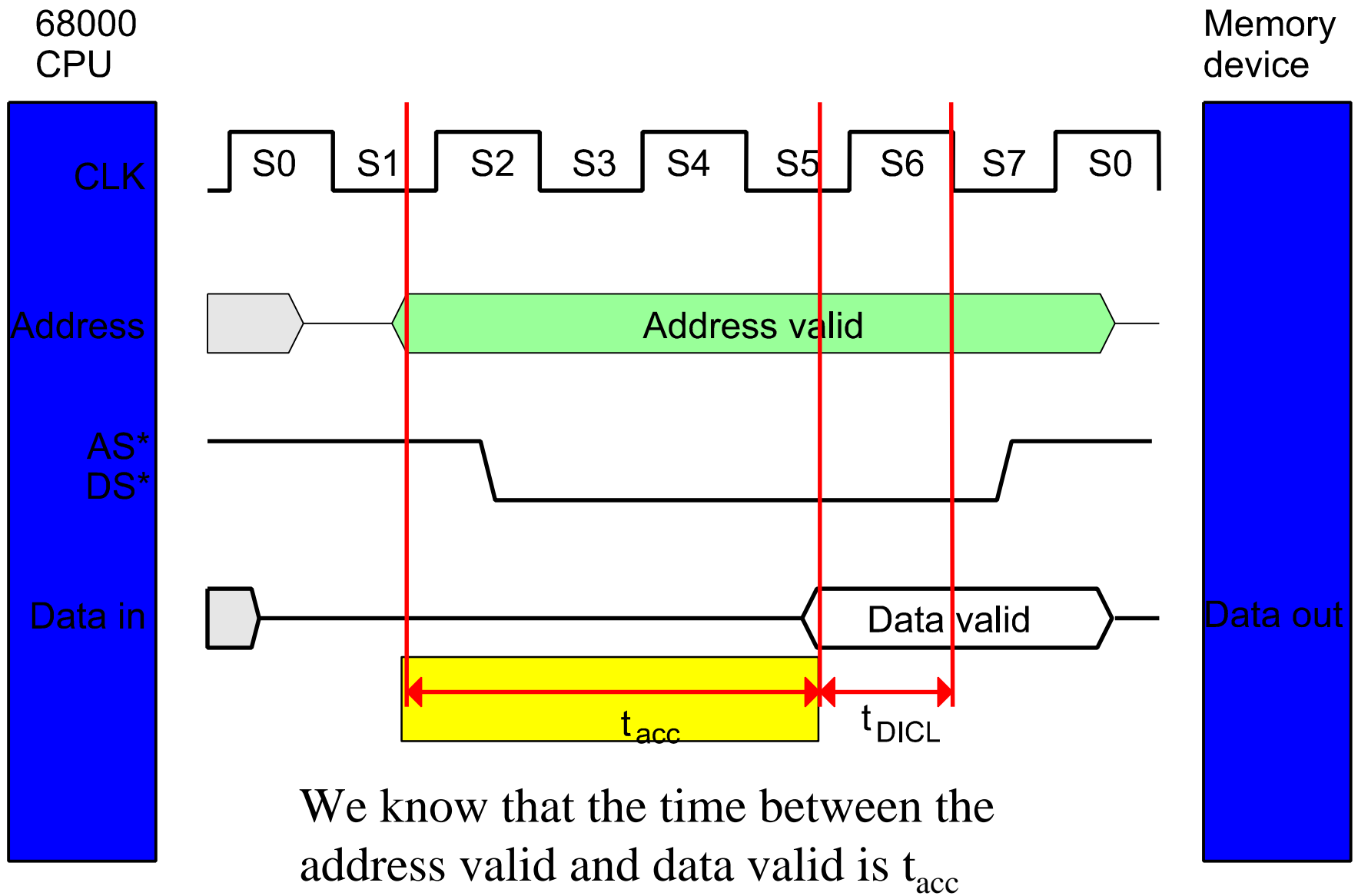

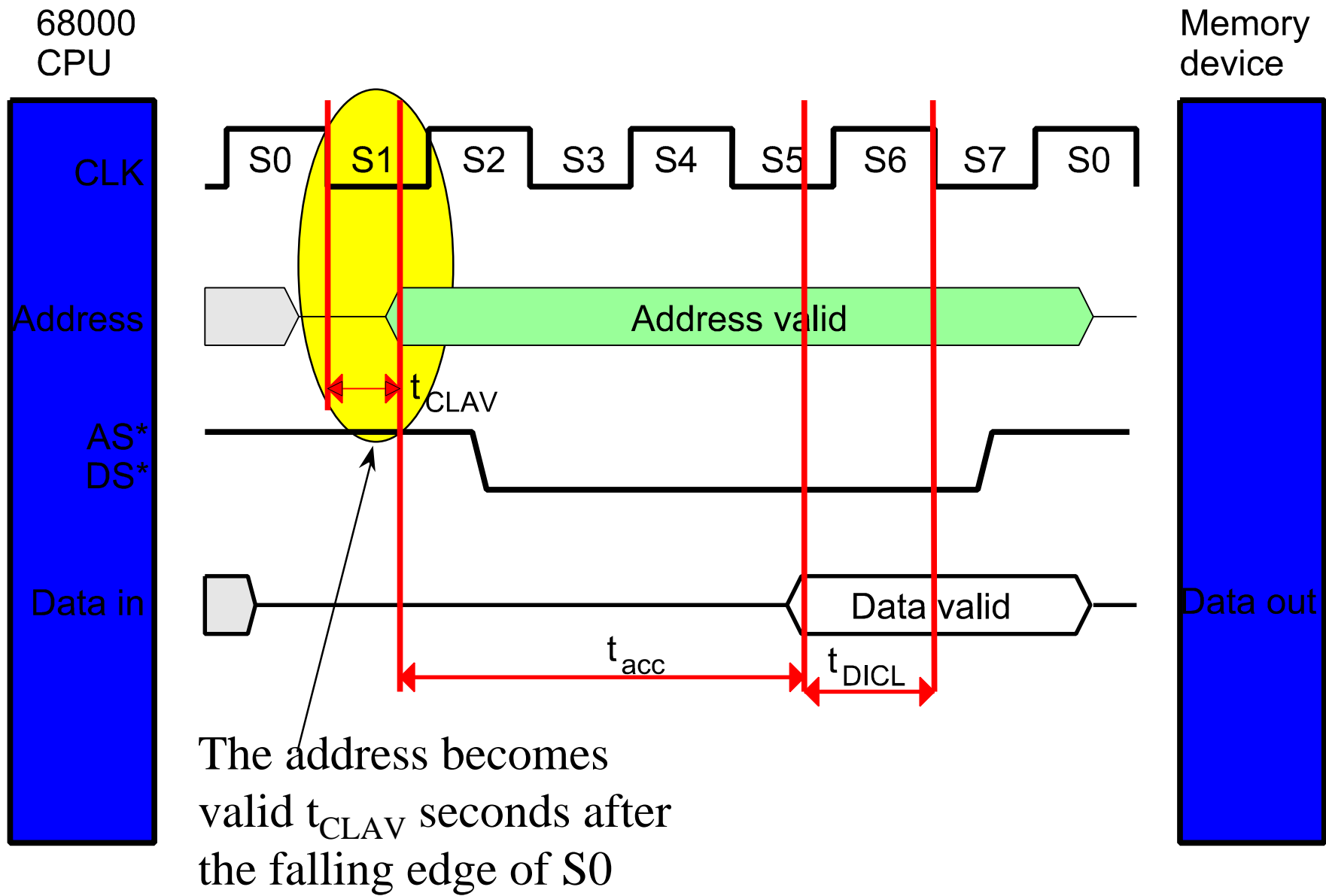

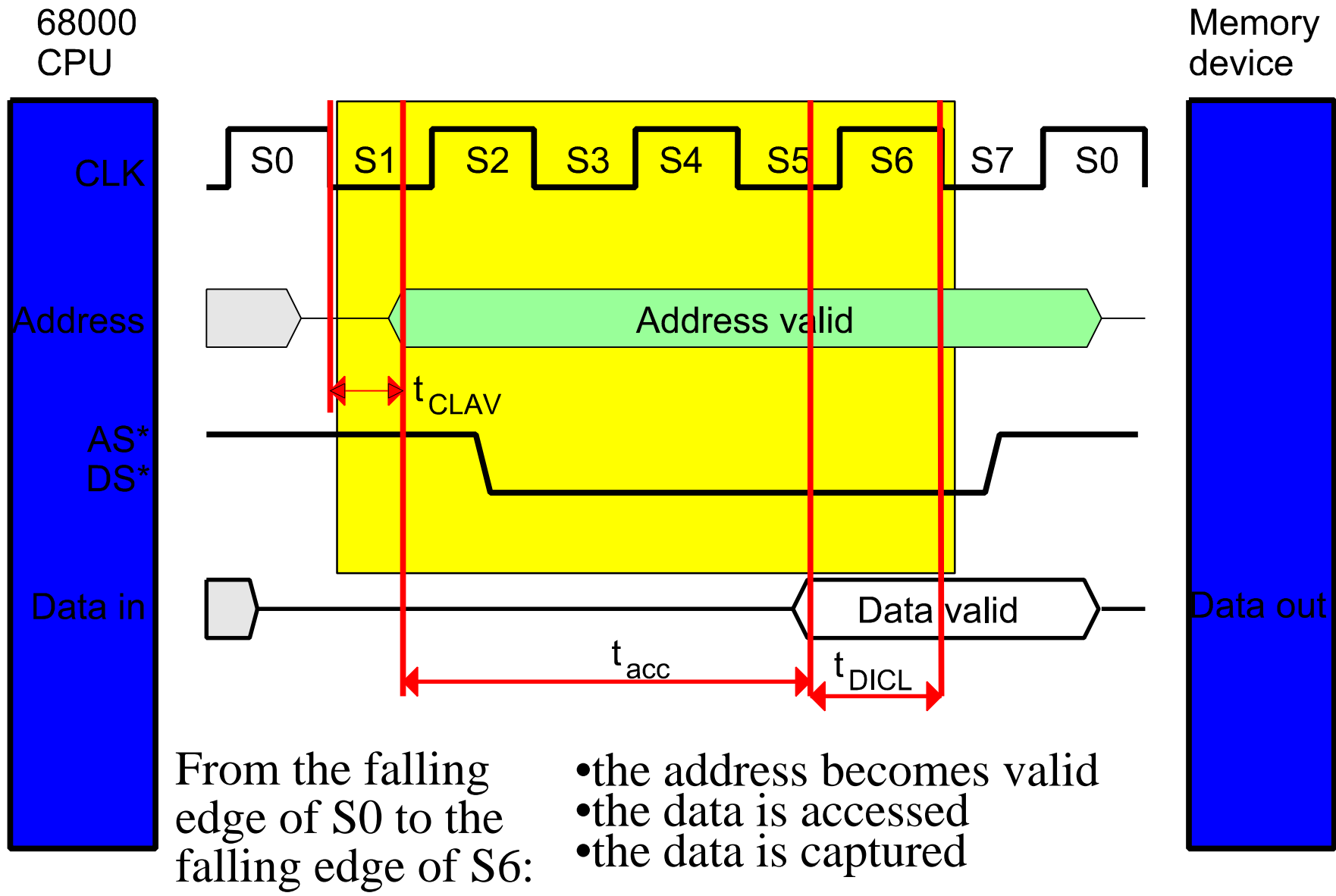

 

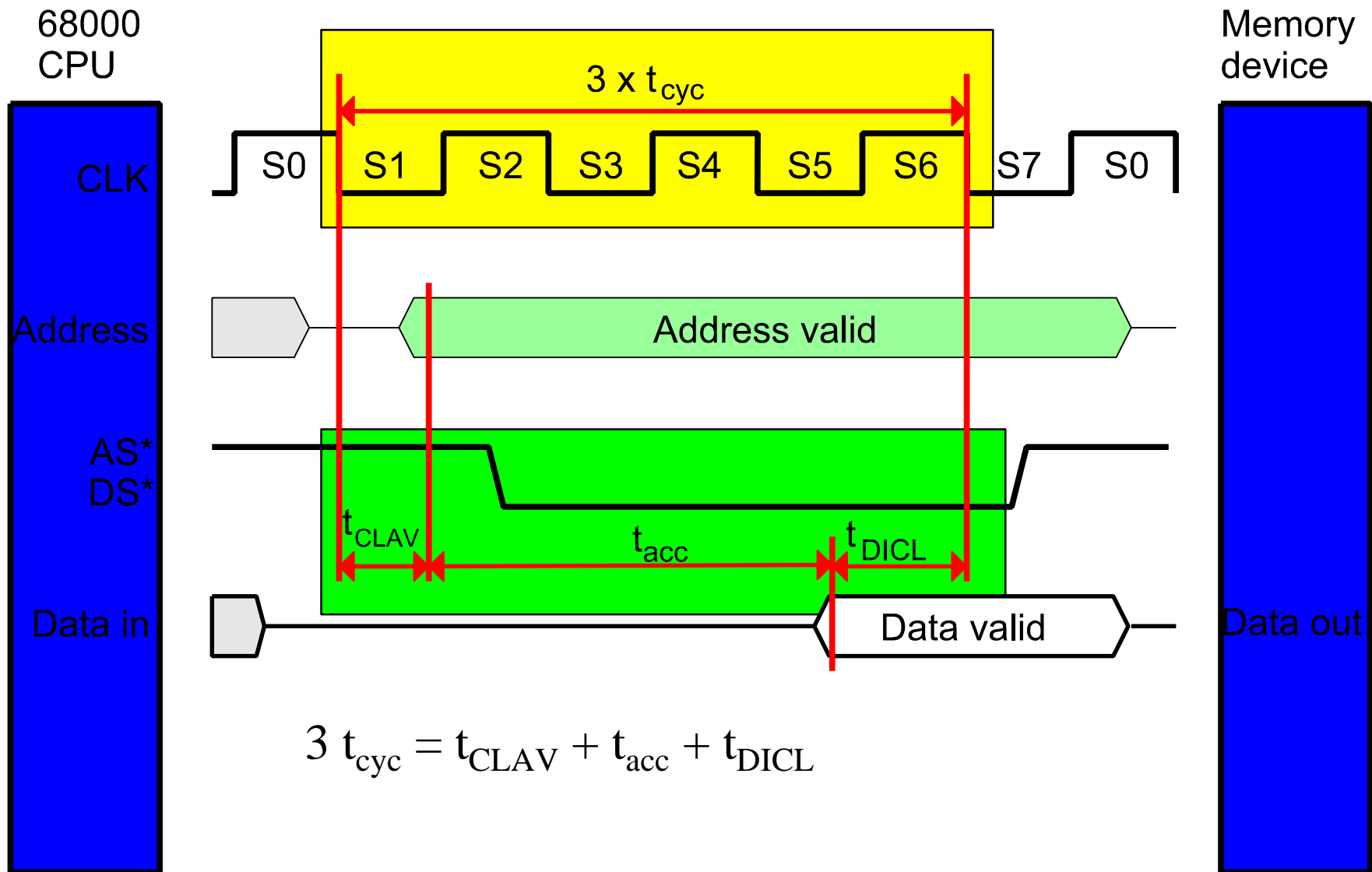

Timing Example

- 68000 clock 8 MHz
 - 68000 CPU
 - 68000 CPU
 - What is the minimum t_{acc} ?
 - $3 t_{CYC} = t_{CLAV} + t_{acc} + t_{DICL}$
 - $375 = 70 + t_{acc} + 15$
 - $t_{acc} = 290 \text{ ns}$
- $t_{CYC} = 125 \text{ ns}$
 $t_{CLAV} = 70 \text{ ns}$
 $t_{DICL} = 15 \text{ ns}$

68000 Synch/Asynch System

- **Timing spec references asynchronous signals for memory actions**
- **Spec references clock for CPU actions**
 - CPU outputs change
 - CPU samples inputs
- **Metastability**
 - what if input changes at same time clock samples it?
 - violates setup and hold time specifications
 - » sometimes result is undefined
 - » sometimes spec says wait a clock cycle
 - in practice input logic can go into *metastable state*
 - » in between 0 and 1
 - » cause other logic to fail
 - design to avoid this situation

68000 Connected to 6116P-6 SRAM

- **Features**

- address decoder to select RAM
 - » 4KB block aligned to 4KB boundary
- use chip select for byte read/write
- optionally delay DTACK

- **Chip select**

Inputs				Outputs		Operation
AS*	RAMCS*	UDS*	LDS*	CS2*	CS1*	
1	X	X	X	1	1	Noop
X	1	X	X	1	1	Noop
0	0	0	0	0	0	Word
0	0	0	1	0	1	Upper byte
0	0	1	0	1	0	Lower byte
0	0	1	1	1	1	Noop

Read Cycle Calculations

- Relate 68000 timing diagram to 6116P diagram
- Memory access
 - S0 fall to S6 fall = $3 \times t_{CYC}$
 - address becomes valid (t_{CLAV}), memory accessed (t_{AA}), data setup (t_{DICL})
 - total memory address access time = $t_{CLAV} + t_{AA} + t_{DICL}$
- Memory read for 8 MHz 68000
 - $3 \times t_{CYC} > t_{CLAV} + t_{AA} + t_{DICL}$
 - $t_{AA} < 3 \times t_{CYC} - t_{CLAV} - t_{DICL}$
 - $t_{AA} < 3 \times 125 - 70 - 15 = 290 \text{ ns}$
 - 6116P has $t_{AA} < 200 \text{ ns}$, so zero wait states
- Memory read for 12.5 MHz 68000
 - $t_{AA} < 3 \times 80 - 55 - 10 = 175 \text{ ns}$
 - need to add a wait state

Read Cycle Calculations (cont.)

- **Data hold time**

- $t_{\text{SHDI}} > 0$ ns from rising AS^*
- address does not change until rising S0
- rising $\text{AS}^*/\text{UDS}^*/\text{LDS}^*$ deselects chip
- deselect to floating (t_{CHZ}) > 0 ns
- gate delays ensure spec

- **Chip select/deselect time**

- CS^* from AS^* , RAMCS^* , $\text{USD}^*/\text{LDS}^*$
- if address decode < 30 ns, then CS^* one gate delay after AS^*
- CS^* to driver on < 15 ns, long before data available
- data bus floated $t_{\text{CLSH}} + t_{\text{GATE}} + t_{\text{CHZ}}$ after S7 starts
 - » if $t_{\text{GATE}} = 10$ ns, bus floats $70 + 10 + 60 = 140$ ns after S7
- S7 , $\text{S0} = 62.5$ ns, bus could float 15 ns into S1
- okay since next access in S2

68000 Write Cycle

- **Similar to read cycle**
- **Difference**
 - CPU puts data on data bus early in bus cycle
 - UDS*/LDS* not asserted until data on bus
 - R/~W is set low
 - » most memory needs address stable before this
 - memory/peripheral reads data
 - » can use UDS*/LDS* to latch data into memory
- **Timing requirements**
 - typically write cycle specs can be easily met
 - memories write faster than they read
 - » big driver to little cell vs. little cell to big load

Read-Modify-Write Cycle

- **Used for indivisible operations**
 - locks, semaphores, monitors
 - TAS - test and set
 - CAS/CAS2 - compare and swap
- **68000**
 - keeps address strobe low
 - address bus value same for read and write
 - strobes data for read and write
 - set R/~W high, then low

68040 & ColdFire Timing

- **Synchronous bus**
 - I/O devices and memory also referenced to clock
- **Much simpler timing**
- **Many fewer clock cycles per bus transaction**
 - Everything referenced to clock
- **See Section 7.5**
- **See ColdFire User's Manual pg. 17-10**